

# LOGICAL ORGANIZATION OF COMPUTER-I

Time : 3 Hours

Maximum Marks : 80

## (Compulsory Question)

1. Attempt all the following :

a) Abbreviate :

BCD, ASCII, PROM

b) A Register stores High, Low, Low, High. Find number in Decimal, Octal and Hexadecimal.

c) Prove NOR is a Universal gate.

d) Make Venn diagram for NOR, AND, NOT gates.

e) Draw and label 3-variable K-Map.

f) Make Truth Table for 8421 code.

## Unit-I

2. a) Convert as follows :

$$(10.625)_{10} \rightarrow ( )_{16}$$

$$(17.3)_{10} \rightarrow ( )_2$$

$$(X)_2 \rightarrow (1AB7)$$

$$(1101110110)_2 \rightarrow ( )_8$$

$$(X)_4 = (768)_{10}.$$

b) Solve using 2's complement

+14

-9

-6

-10

-10

-16

3. a) Define Floating point Representation. Also discuss Overflow and Underflow in floating arithmetic using example.
- b) Write notes on the following :
- Error Detection and Correction
  - Self-complementing code.

### Unit-II

4. a) Differentiate between Ordinary and Boolean Algebra, and write postulates of Boolean Algebra.
- b) Solve using Boolean Algebra

$$(X + Y)(XZ + Z)(\overline{Y + XZ}) = \overline{X}YZ$$

- c) Find SOP, POS for Full-adder.
5. a) Solve using K-Map :

$$Z(A, B, C, D) = \sum (0, 2, 8, 10, 15)$$

$$Z(A, B, C) = \sum (0, 1, 2) + \sum_{\phi} (6, 7)$$

$$Z(A, B, C, D) = \pi (0, 2, 4, 6, 8, 10, 12, 14)$$

- b) State and prove Demorgan's Law for 3-variables.

### Unit-III

6. a) Define Logic, and explain AND, NOR, NAND gates for 3 variables.

- b) Explain Half-Adder using NAND gates only.
7. a) Write a note on AND-OR-INVERT.  
b) Implement using NOR gate only :

$$F = (A+B) (C+D)E$$

$$X = (A\bar{B} + \bar{A}B)(C + \bar{D}).$$

#### Unit-IV

8. a) Explain 4 to 10 Line decoder.  
b) Make circuit for Comparator.
9. Write notes on the following :
- i) 8421 to 2421 Code convertor.
  - ii) 7-segment Display unit.