

Roll No. 0006008748

Total Pages : 03

BCA/D-17

1230

LOGICAL ORGANIZATION OF
COMPUTER-I
BCA-114

Time : Three Hours]

[Maximum Marks : 80

Note : Attempt *Five* questions in all, selecting *one* question from each Unit. Q. No. 1 is compulsory.

1. (a) How many control signals are needed for 8:1 and 16:1 MUX ? 2
- (b) Prove that NAND is universal gate. 2
- (c) State and prove DeMorgan's laws. 4
- (d) Make TT for cyclic code and excess-3 code from 0 to 9. 4
- (e) Solve using Boolean Algebra :
 - (i) $a + a.b = a$
 - (ii) $a + \bar{a}.b = (a+b)$. 4

Unit I

2. (a) Perform conversions :
 - (i) $(13.625)_{10} \rightarrow ()_2$ 2
 - $\rightarrow ()_{16}$

(2-01/6) L-1230

P.T.O.

- (ii) $(X)_4 = (1234)_4$ 2
- (iii) $(101111001101)_2 \rightarrow ()_{16}$ 2
- (iv) $(3A37) \rightarrow ()_2$ 2
 $\rightarrow ()_8$ 2
- (b) What is Error Detection and correction coding scheme ? 4
- (c) Write abbreviation for ASCII, EBCDIC, BCD, DRAM. 4
3. (a) Perform using 2's compliment : 6
- | | | |
|------------|------------|-----------|
| -9 | +32 | -6 |
| <u>-10</u> | <u>-17</u> | <u>-7</u> |
- (b) Explain concept of floating point representation using condition of overflow and underflow. 10

Unit II

4. (a) Define Boolean Algebra and write its postulates. 8
- (b) Solve using boolean algebra : 8
- $$XY + \bar{X}Z + YZ = XY + \bar{X}Z$$
- $$(X + Y) (Z) (\bar{Y} + XZ) = \bar{X}YZ$$
5. (a) Draw and label 4 var K-Map. 4
- (b) Make Venn diagram for OR and AND Gates. 4

- (c) Solve using K-map :

$$Z = \sum 0, 2, 8, 10, 12 + \sum_{\phi} 4, 6, 14, 15$$

$$Z = \sum 0, 1, 4, 10, 15 + \sum_{\phi} 5, 11, 14 \quad 8$$

Unit III

6. (a) Define and explain the following gates : 6

NOR, XOR, NOT.

- (b) Define and explain the following gates using 3-variables TT :
AND, NAND, OR. 6

- (c) Make circuit : 4

$$(X\bar{Y} + \bar{X}Y)CD + (\bar{X}\bar{Y} + XY)\overline{CD}$$

7. Explain combinational logic, its characteristics and design procedures. 16

Unit IV

8. (a) Make 4 : 1 MUX.
(b) Draw code convertor from 8421 to 2421. 16

9. (a) Make full-adder using K-map.
(b) Draw 4 to 10 line decoder. 16