

Roll No. ....

Total Pages : 3

BCA/D-16

856

LOGICAL ORGANISATION OF COMPUTER – I

Paper : BCA-114

Time : Three Hours]

[Maximum Marks : 80

**Note :** Attempt any *five* questions. Question No. 1 is compulsory.  
Attempt remaining *four* questions selecting *one* from each unit. All questions carry equal marks.

**Compulsory Question**

1. (i) Explain Minterm.  
(ii) Define Involution law of Boolean Algebra.  
(iii) Prove Distributive law using Venn Diagram.  
(iv)  $(1100.001)_2 = (?)_{10}$ .  
(v) What is NAND gate ?  
(vi) What is Combinational circuit ?  
(vii) What is Multiplexer ?  
(viii) Why computer system uses binary number system ?  
(2×8=16)

**UNIT-I**

2. (i) What is Number system ? Explain two positional number systems. 8  
(ii)  $(FA)_{16} = (?)_2 = (?)_{10} = (?)_8 = (?)_5$ . 8

856/4,300/KD/229

[P.T.O.]

3. (i) Discuss how negative numbers can be represented in computer system. 8
- (ii) Explain ASCII and EBCDIC Code. 8

### UNIT-II

4. (i) State De Morgan's Theorem and prove it. 8
- (ii) Explain two Canonical forms of Boolean Expression for a truth table of your choice. 8

5. (i) Simplify the Boolean function 8

$$F(x, y, z, u) = \sum(0, 2, 4, 6, 9, 13, 15) + \sum_{\phi}(1, 3, 7)$$

- (ii) Examine the validity of following Boolean equation

$$XZ + Y\bar{X} + YZ = \bar{X}Z + \bar{Y}X$$

and also draw circuit diagram of L.H.S. using NAND gate. 8

### UNIT-III

6. (i) Simplify the following Boolean expression and implement it using OR and AND gates : 8

$$Y = \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} + A\bar{B}C\bar{D}$$

- (ii) Explain the working of 3 input NAND gate. 8

7. (i) Explain implementation of AND, OR, NOT gates by NOR gate. 8

- (ii) Prove that NAND gate is an universal gate. 8

#### UNIT-IV

8. (i) Describe the design procedures of Combinational circuit with an example. 8
- (ii) What is Full Adder ? Explain it. Draw its logic diagram by using Half Adder. 8
9. (i) Explain and draw the logic diagram of decimal to BCD encoder. 8
- (ii) Design a  $6 \times 32$  decoder with the help of  $3 \times 8$  decoder. 8
-