

Logical Organisation of Computer-I

Time : Three Hours

Maximum Marks : 80

Note : Attempt *five* questions in all. Select *one* question from each section.

Question No. 1 is compulsory.

(COMPULSORY QUESTION)

- | | | | |
|----|-----|--|---|
| 1. | (a) | Write the full form :
ASCII, EBCDIC, DRAM. | 3 |
| | (b) | Make Truth table for 3 variable AND, NOR gate. | 3 |
| | (c) | Prove that NAND is a universal gate. | 3 |
| | (d) | State & prove Demorgan's law. | 3 |
| | (e) | Make Venn diagram for OR, AND, NOR gates. | 3 |
| | (f) | Define Duality principle. | 1 |

UNIT-I

- | | | | |
|----|-----|--|----|
| 2. | (a) | Convert as directed : | |
| | | $(7.3)_{10} \rightarrow ()_2$ | |
| | | $(10.625)_{10} \rightarrow ()_8$ | |
| | | $(X)_3 \rightarrow (1234)_{10}$ | |
| | | $(AF3D)_{16} \rightarrow ()_2$ | |
| | | $(117.6C)_{16} \rightarrow \text{Octal}$ | 10 |
| | (b) | Use 2's complement to solve | |
| | | $-6 \qquad \qquad -42 \qquad \qquad -9$ | |
| | | $-8 \qquad \qquad +30 \qquad \qquad -4$ | 6 |

3. (a) Explain Floating point representation. 8
 (b) Write a note on 2421, cyclic code. 4
 (c) Perform BCD addition for 9+6 4

UNIT-II

4. (a) Define Boolean Algebra & write its postulates. 8
 (b) Solve using Boolean Algebra:

$$XY + \overline{X}Z + YZ = XY + \overline{X}Z$$

$$ABC + \overline{A}\overline{B}C + A\overline{B}\overline{C} + \overline{A}B\overline{C} = A$$

5. (a) Solve using K-map 4

$$Z = \sum 0, 2, 3, 7, 9 + \sum 1, 4, 5, 11$$

$$Z = \pi 0, 2, 4, 6$$

- (b) Prove using Truth table 4

$$A \oplus (B \oplus C) = (A \oplus B) \oplus C$$

- (c) Draw and label 4 variable K-map. 4

UNIT-III

6. (a) Define Logic and explain NAND, XOR, OR gates. 8
 (b) Draw circuits:

$$(i) X = (\overline{A}B + A\overline{B})CD + \overline{X}YZ$$

$$(ii) P = (AB + \overline{A}\overline{B})\overline{CD} + (\overline{A} + \overline{B})\overline{C}\overline{D}$$

7. (a) Write note on AND-OR-INERT using example. 8
 (b) Explain Multilevel realization using NAND gates.

UNIT-IV

8. (a) Explain 4:1 multiplexer. 16
 (b) Draw 10 to 4 Line Encoder.
 9. (a) Explain 8421 to Cyclic code converter. 16
 (b) Make 7-segment display unit.