

Roll No.

Total Pages:
10417

MCA/D-12
COMPUTER ORGANISATION
Paper-MCA-102

Time allowed: 3 hours

Maximum marks: 80

Note: Attempt five questions in all. Question no. 1 is compulsory.
Attempt four more questions selecting one question from each unit.

Compulsory Question

1. Answer the following questions in brief: 8x3=24
- (a) Draw the truth table for three-input equivalence gate.
 - (b) State three-variable DeMorgan's laws.
 - (c) What is flash memory? Enumerate its applications.
 - (d) What is flip-flop? What are limitations of JK flip-flop?
 - (e) What is zero address instruction formats? Explain its application.
 - (f) If main memory size is 256MW and word size is 32 bit then compute the size of MAR and MBR.
 - (g) Implement $f = X'Y + X'Y + Z$ using (i) NAND gates, and (ii) NOR gates.
 - (h) Why can't you connect I/O devices directly with a system bus?

Unit-I

2. (a) Represent 73_{10} in 1's complement, ternary, duo-decimal, BCD code, ASCII, Unicode and EBCDIC code. 7
- (b) What is error correcting code? Design single error detecting and single-error correcting Hamming code for excess-3 BCD code. 7
3. (a) Simplify $Z(Y+Z)(X+Y+Z)$ by using Boolean algebra. 4
- (b) Convert $(A+B)(B+C)$ into canonical forms. 4
- (c) Explain Booth multiplication by giving an example. 6

Unit-II

4. (a) What is Full subtractor? Draw its truth table. Design it by using half subtractors. 7
- (b) Implement $Y = (A+B+C)(D+E)F$ using OR-AND logic and using NOR-NOR Logic. 7
5. (a) What is combinational circuit? Design decimal to BCD encoder. 7
- (b) Design 4x16 line decoder using two 3x8 line decoders. 7

Unit-III

6. (a) What is Edge-triggered flip-flop? Explain the construction and working of D-type edge Triggered flip-flop. 7
- (b) Design a module-10 counter using JK flip-flop. 7
7. (a) Draw a circuit diagram of SRAM binary, cell. Explain read and write operations on it. Also, differentiate between SRAM and DRAM. 7
- (b) What is CD-ROM? Explain construction and working of CD-ROM. 7

Unit-IV

- | | |
|---|---|
| 8. (a) Explain various displacements based addressing modes? | 7 |
| (b) Explain instruction cycle of a computer system with the help of a flow chart. | 7 |
| 9. Write short note on the following: | |
| (a) Microprogram Sequencer. | 7 |
| (b) IOP. | 7 |