

from its elements.

Paper : II Logical Organization of Computer

(Compulsory Question)

1.
 - (a) What is the difference in triggering Flip-Flop during Pulse Duration and Pulse Transition ?
 - (b) What is difference between Latch and Register ?
 - (c) What is purpose of Bidirectional Shift Register ?
 - (d) Differentiate between Harddisk and CD ROM.
 - (e) What is difference between High level language Instruction and Machine Instruction ?
 - (f) Differentiate between direct and Indirect Addressing mode.

$$6 \times 3 = 18$$

UNIT-I

2.
 - (a) What is problem in RS Flip-Flop ?
 - (b) Explain the working of D-type and T-type Flip-Flop and also show its characteristic table and equation. 6, 12
3.
 - (a) What is Race condition in J-K Flip-Flop ?

- (b) Draw the logic Diagram of J-K master slave Flip-Flop and explain its working. 6, 12

UNIT-II

4. What is Register ? Design a 4 bit Parallel in Serial Out (PISO) Register and explain its working. 18
5. What is Synchronous Counter ? Design a MOD-5 counter. 18

UNIT-III

6. What is RAM ? Design a 16 words 3 bit/word RAM. 18
7. What is Optical Disk ? What are its types ? How data is recorded and read in CD ROM ?

UNIT-IV

8. (a) Write Assembly Language instruction to compute $X = (A + B) * (C + D)$ for computer which uses 2 Address, one Address and zero Address instruction Format.
- (b) What are Register reference Instructions ? Give example.

UNIT-V

9. (a) Explain I/O transfer using DMA.
- (b) What is purpose of IOP ? Explain its operation. 10, 8