

Logical Organization of Computer - 1

Time : Three Hours]

[Maximum Marks : 90

1. (a) Represent the Decimal number 492 in BCD code.
- (b) Write short note on ASCII code.
- (c) Find the dual of expression : $a + (\bar{a}.b)$
- (d) State and prove Demorgan's law.
- (e) Why NAND is termed as universal gate?
- (f) Represent the Boolean expression $x + Y.\bar{Z}$ with the help of NOR gate only.
- (g) Design truth table for full-adder.
- (h) What is Multiplexer? 20

UNIT - I

2. (a) Explain fixed and floating - point representation of numbers with the help of examples. 10
- (b) Perform the following algorithm operation using 2's complement representation for negative numbers.
 $(58)_{10} - (33)_{10} + (14)_{10} + (-45)_{10}$ 5
- (c) Determine the value of base b if $(16)_{10} = (100)_b$. 5

3. (a) Determine which bit, if any, is in error in the even parity. Hamming coded character is 1100111. Decode the message. 10
- (b) Represent the decimal number 678.7 in
 (i) binary (ii) Excess - 3 code
 (iii) Gray code (iv) ASCII Code 10

UNIT - II

4. (a) Convert the SOP equation, $F = A\bar{B}C + \bar{A}BC$ into its POS form. 10
- (b) Prove that $xy + \bar{x}\bar{y} + \bar{x}yz = xy\bar{z} + \bar{x}\bar{y} + yz$ with the help of truth table. 10
5. (a) Simplify $ABC + \bar{A}BC + AB\bar{C} + \bar{A}BC + \bar{A}\bar{B}\bar{C}$ using K-map. 10
- (b) Simplify the following three variable expression using Boolean algebra $F = \Sigma m(1,3,5,7)$. 10

UNIT - III

6. (a) Simplify the following Boolean equation and realize the same using logic gates 10

$$F = (\bar{A} + B)(A + \bar{C})(\bar{B} + \bar{C})$$

- (b) Simplify the following logic expression and realize it using NAND gates. 10

$$F = A\bar{B} + ABC\bar{C} + ABCD + ABC\bar{D}$$

7. (a) Write and explain design procedure of combinational circuits with the help of an example. Implement the function using. 10
- (i) NAND gates and 10
- (ii) NOR gates only 10
- (b) $F = A.B + \bar{C} + D.E$. 10

UNIT - IV

8. Explain Full-Subtractor in detail. 20
9. Explain 2-bit magnitude comparator in detail. 20

